

PHYSICAL COMPUTING

WEEK 04

Inductive Load

Anything with a coil and a magnet


Inductive vs Resistive loads

- 1) Inductive loads use magnetic fields. Examples - Motors, solenoids, and relays. If it moves, it's probably an inductive load.
- 2) Inductive loads can cause blowback voltage. Circuits should be protected from this by diodes.
- 3) Blowback is caused by a surge of voltage created by the collapsing magnetic field in an inductor.
- 4) Resistive loads convert current into other forms of energy, such as heat. No risk of blowback.

Diode Protection

Anything with a coil and a magnet

- Reverse polarity protection.

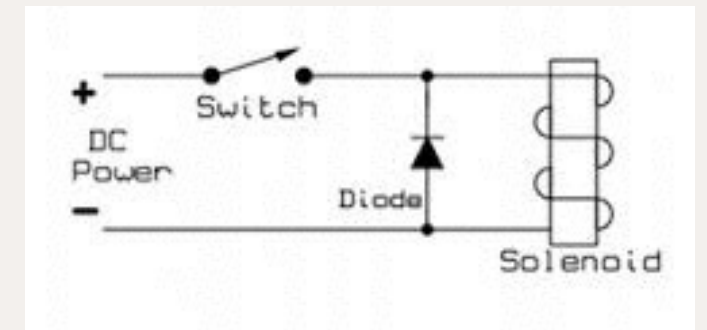



- Reverse-biased diode in parallel with an inductive load. Snubs the blowback current generated by the collapsing magnetic field.

Transistor

Allows a smaller current to control a larger current


Transistor as switch

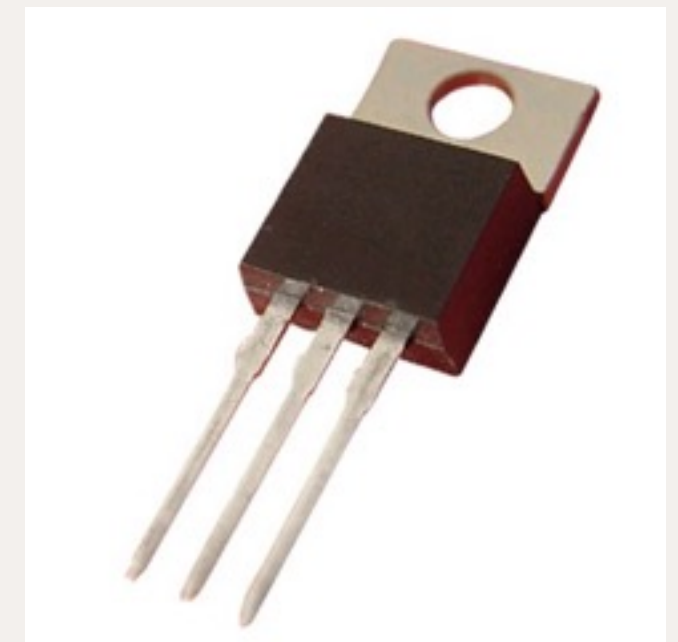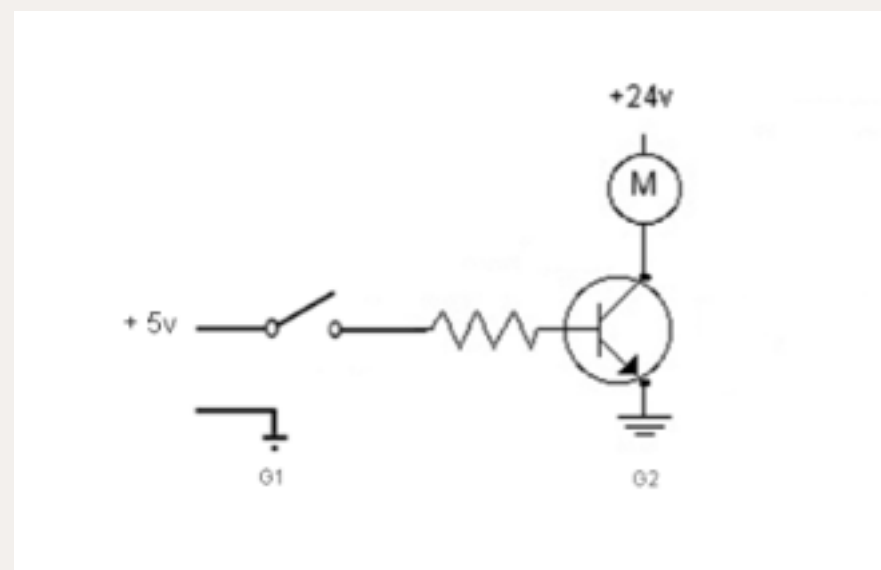
- 1) Most sensors, processors, microcontrollers can't source enough power to make things happen in the real world.
- 2) Transistors allow a large amount of current to be controlled by a small change in voltage.
- 3) Grounds between control circuit and transistor must be common.



Relay

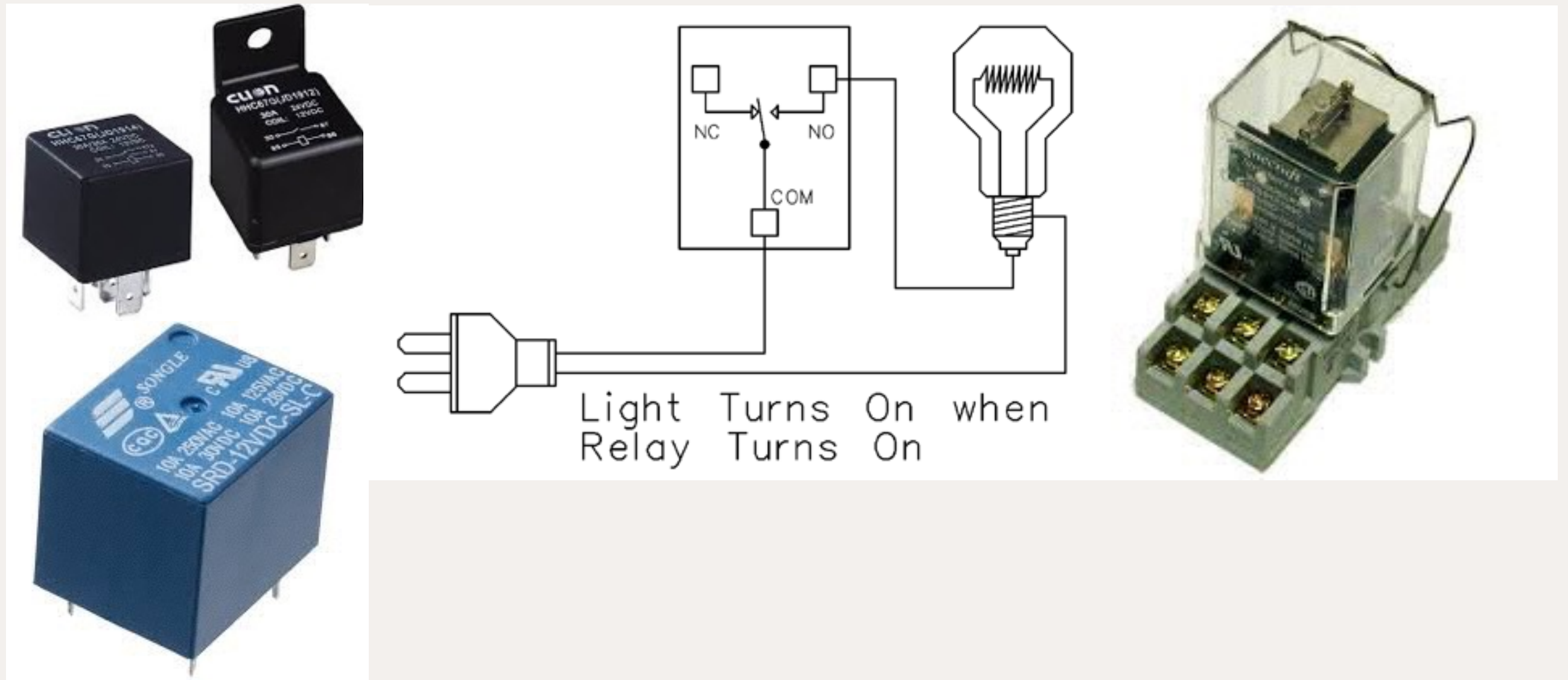An electronically controlled magnetic switch




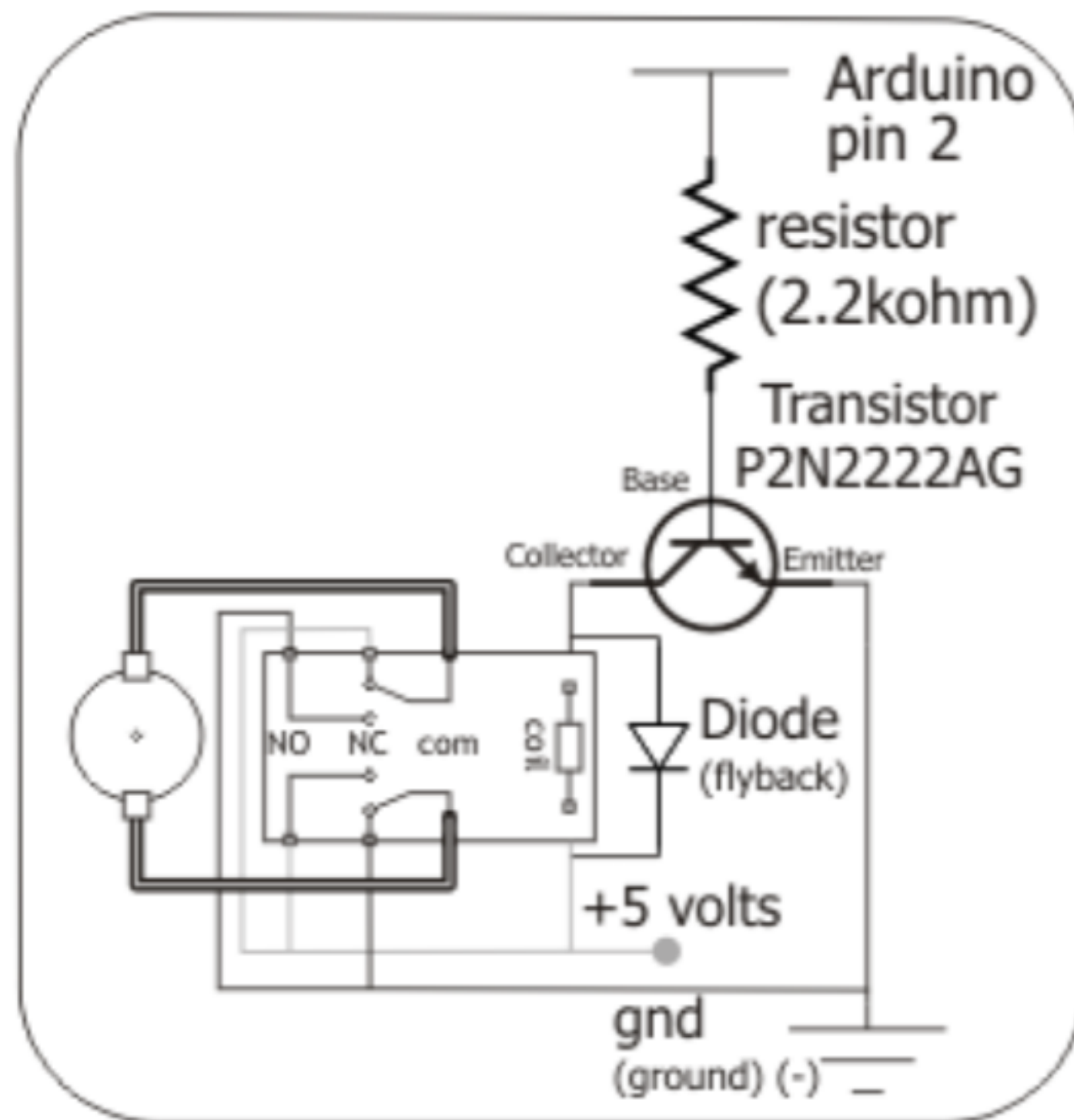

Low current load

Use this type of circuit for low current loads only

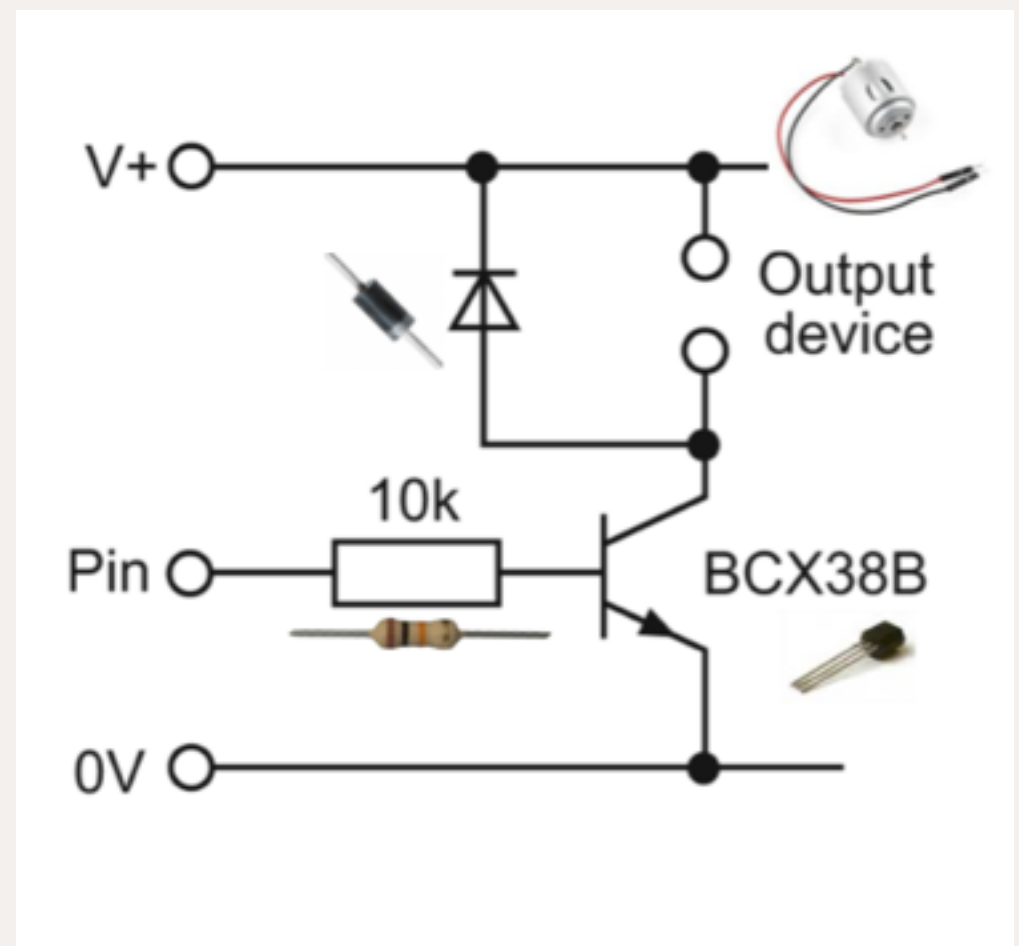BCX38B darlington or other NPN transistor
(uyp to 60V, 800mA, power: 1 WaB)




High current load

Use this type of circuit for high current loads only

Use a heat sink for high currents (see how warm the tab gets, during use)

IRF530 power MOSFET(up to 14A 100V!)

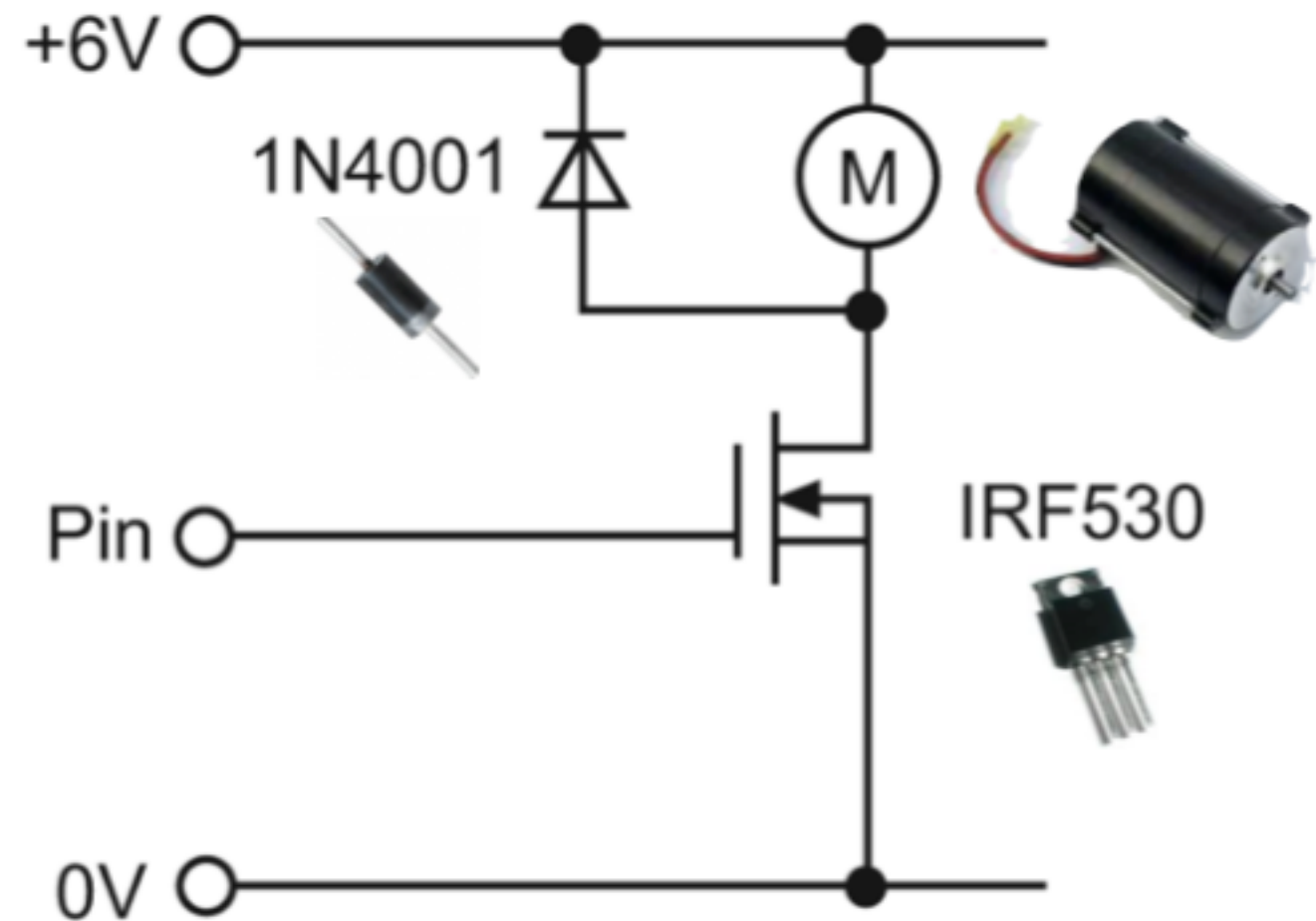

$$P = I(\text{to the})^2 R$$

Symbols for Components



Wires crossing – no contact



Junction (wires joined)




Junction



Switch (normally open)




Switch (normally closed)

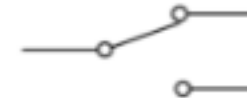

Two-way switch



Single cell

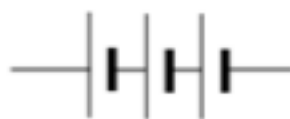


Battery of three cells




Power supply (DC)



Power supply (AC)

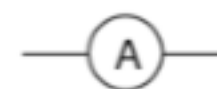


Ammeter

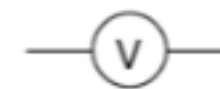


Voltmeter




Resistor

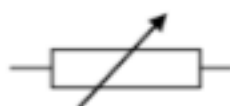


Variable resistor

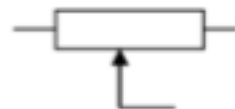

Variable resistor or potentiometer

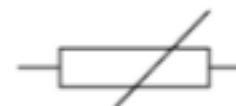

Thermistor

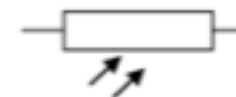

Light dependent resistor (LDR)



Fuse




Earth



Diode




Light-emitting diode (LED)

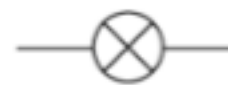

(Signal) lamp



Filament lamp

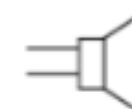

Loudspeaker




Electric bell



Buzzer



Microphone

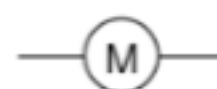

Motor



Generator





Transformer

Capacitor

Stores electrical current for a duration

Measured in Farads.

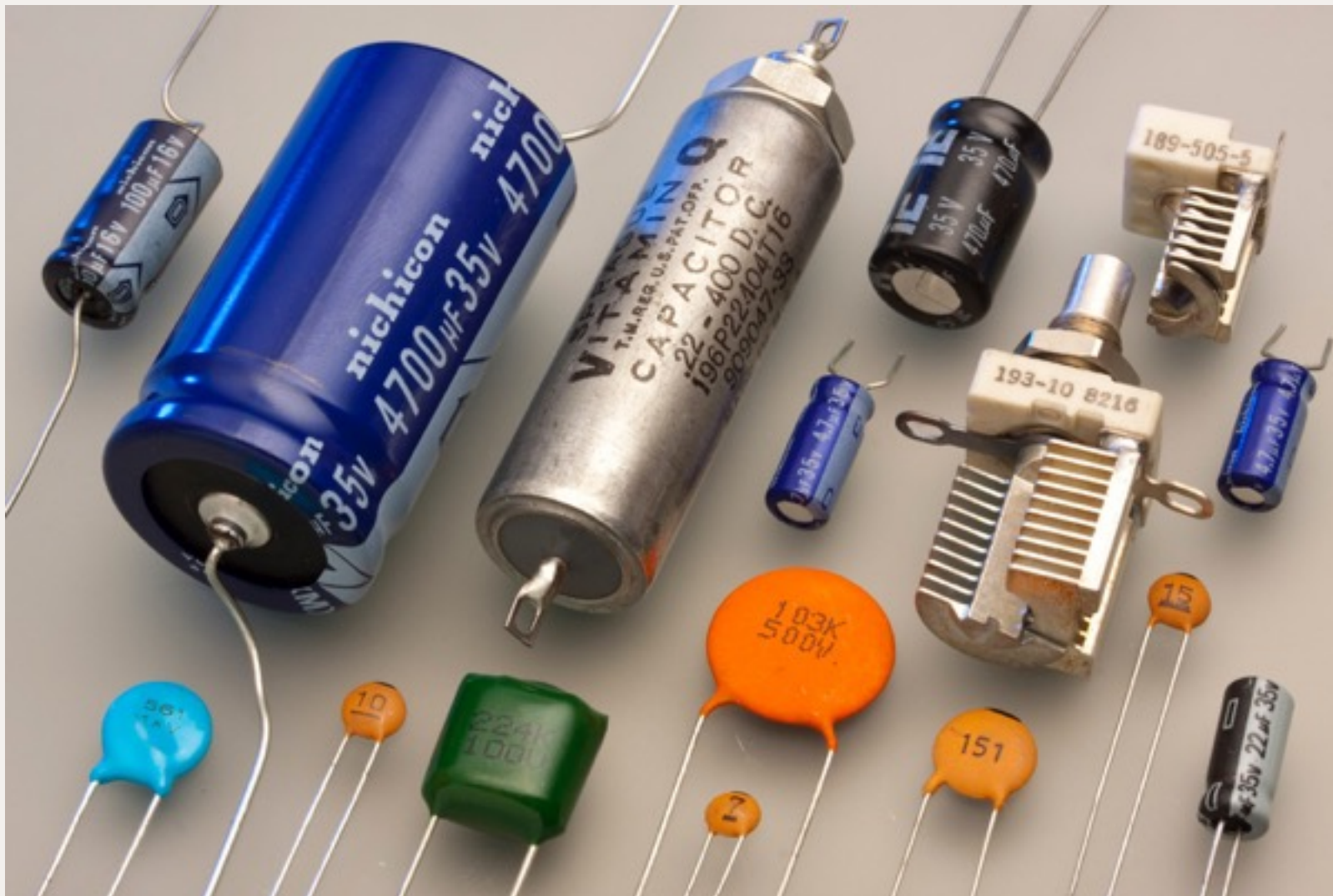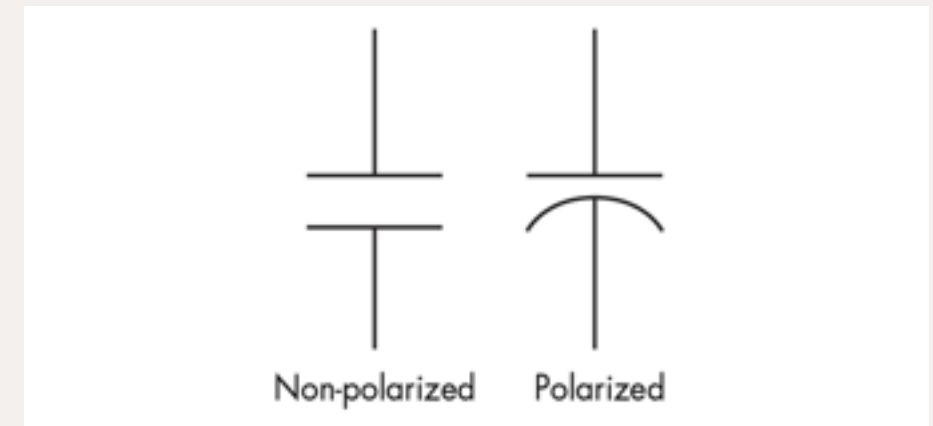Typical capacitance values range from about 1 pF
(10⁻¹² F) to about 1 mF (10⁻³ F).





Capacitor


Has two sides - two “plates” and when enough charge builds up a current flows between them.

Can serve to regulate uneven current flow

This is you, the carpet and your childhood friends.

You can measure this with your arduino. For more info see here:
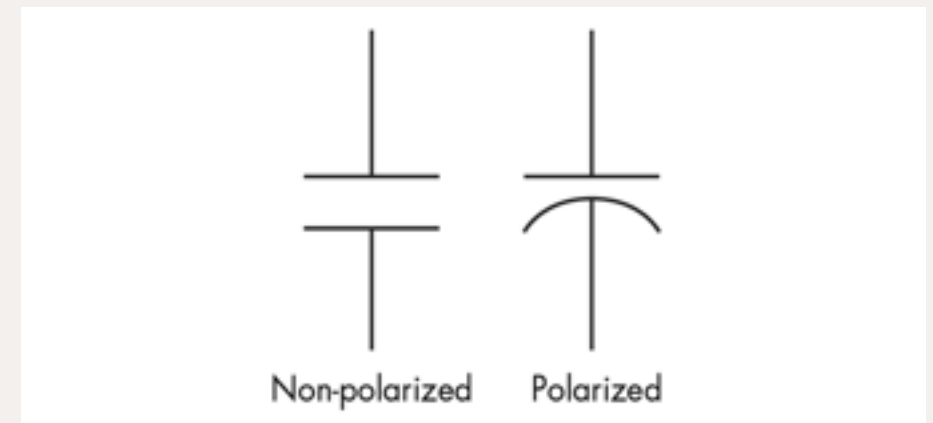
<https://www.youtube.com/watch?v=ZYH9dGl4gUE>



MPR121 breakout

